

**** Disclaimer: This lab write-up is not to be copied, in whole or in part, unless a proper reference is made as to the source. (It is strongly recommended that you use this document only to generate ideas, or as a reference to explain complex physics necessary for completion of your work.) Copying of the contents of this web site and turning in the material as “original material” is plagiarism and will result in serious consequences as determined by your instructor. These consequences may include a failing grade for the particular lab write-up or a failing grade for the entire semester, at the discretion of your instructor. ****

Lab 5: Capacitors

Name: _____

PES 216 Report

Lab Station: _____

Objective

The purpose of this lab was to determine how to measure the capacitance of a capacitor and how capacitors function in series and parallel in a circuit according to Kirchhoff's Rules.

Data and Calculations

Part A – Measuring Capacitance:


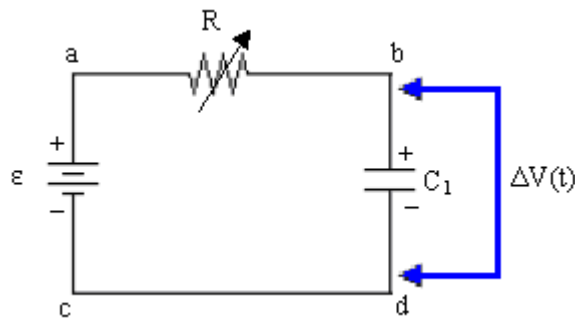


Figure 1: Schematic of the RC circuit built to measure the actual capacitance of provided capacitors.

Part B1 – Big Red Capacitor:

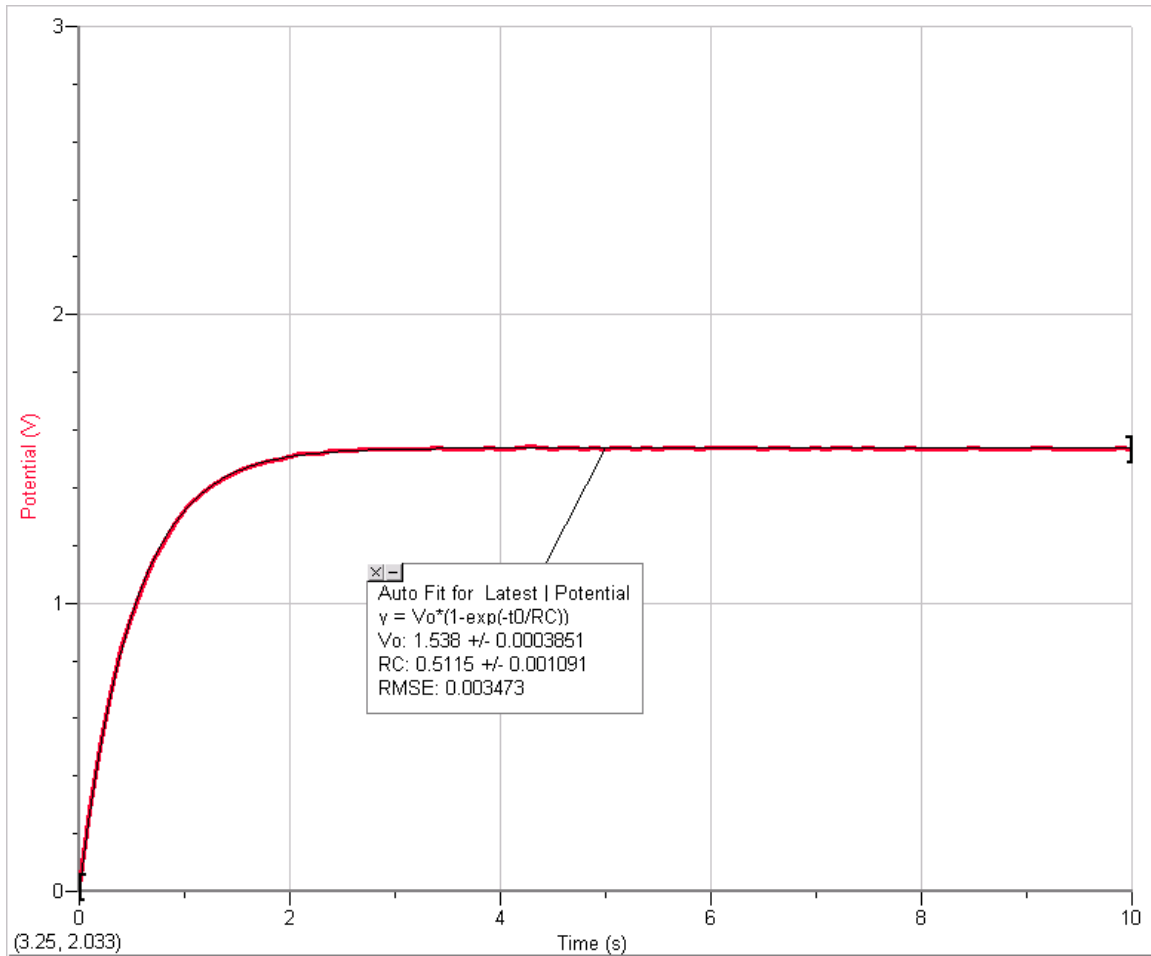

We used Logger Pro to provide a best-fit line for the data captured during the charging of the capacitor.

$$'Potential' = V_o * (1 - \exp(-t0 / RC))$$

Vo [volts]	RC [sec]
1.538 +/- 0.0003851	0.5115 +/- 0.001091

During the experiment it was noted that the resistance substitution box used in the circuit was set to the following resistance:


Resistance [ohms]
400 MΩ

$$C = \frac{0.5115 \text{ sec}}{400000 \Omega} = 1.27875 \mu F$$

$$\% - \text{difference} = \frac{C_{\text{Theory}} - C_{\text{Measured}}}{C_{\text{Theory}}} \times 100\%$$

$$\% - \text{difference} = \frac{1.00 \mu\text{F} - 1.27875 \mu\text{F}}{1.00 \mu\text{F}} \times 100\% = 27.875\%$$

Part B2 – Small Orange Capacitor:

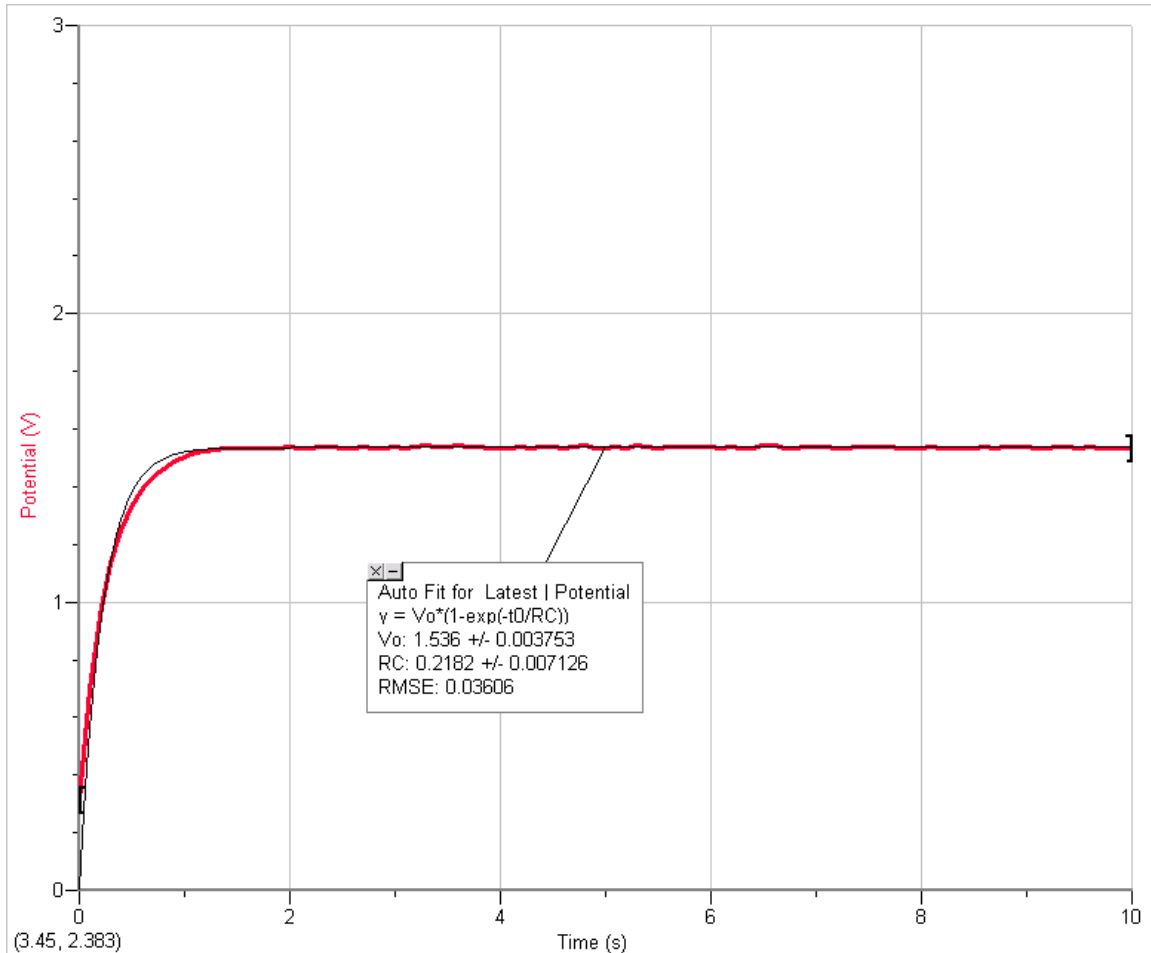

We used Logger Pro to provide a best-fit line for the data captured during the charging of the capacitor.

$$'Potential' = V_o * (1 - \exp(-t0 / RC))$$


Vo [volts]	RC [sec]
1.538 +/- 0.0003851	0.2182 +/- 0.007126

Resistance [ohms]
400 MΩ

$$C = \frac{0.2182 \text{ sec}}{400000 \Omega} = 0.5455 \mu\text{F}$$

$$\% - \text{difference} = \frac{0.56 \mu F - 0.5455 \mu F}{0.56 \mu F} \times 100\% = 2.589\%$$

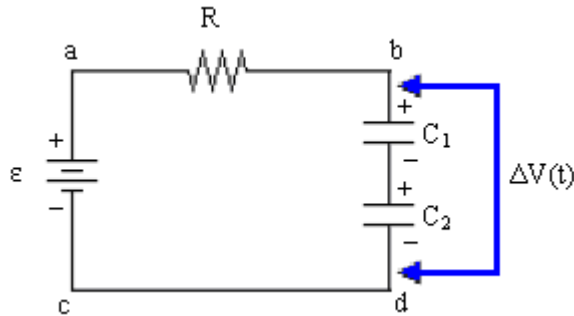Part B – Capacitors in Series and Parallel:




Series: $C_T = \left[\frac{1}{C_1} + \frac{1}{C_2} \right]^{-1}$

Using the values from Part A that we measure, theoretically the total capacitance for the two capacitors in series should be:

$$C_T = \left[\frac{1}{1.27875 \mu F} + \frac{1}{0.5455 \mu F} \right]^{-1}$$

$$C_T = 0.3824 \mu F$$

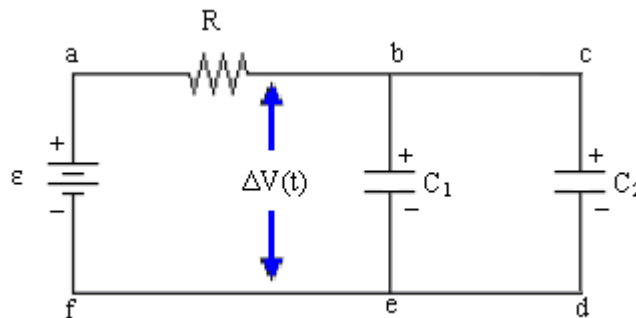


Parallel: $C_T = C_1 + C_2$

Using the values from Part A that we measure, theoretically the total capacitance for the two capacitors in parallel should be:

$$C_T = 1.27875 \mu F + 0.5455 \mu F$$

$$C_T = 1.82425 \mu F$$

Part B1 – Capacitors in Series:

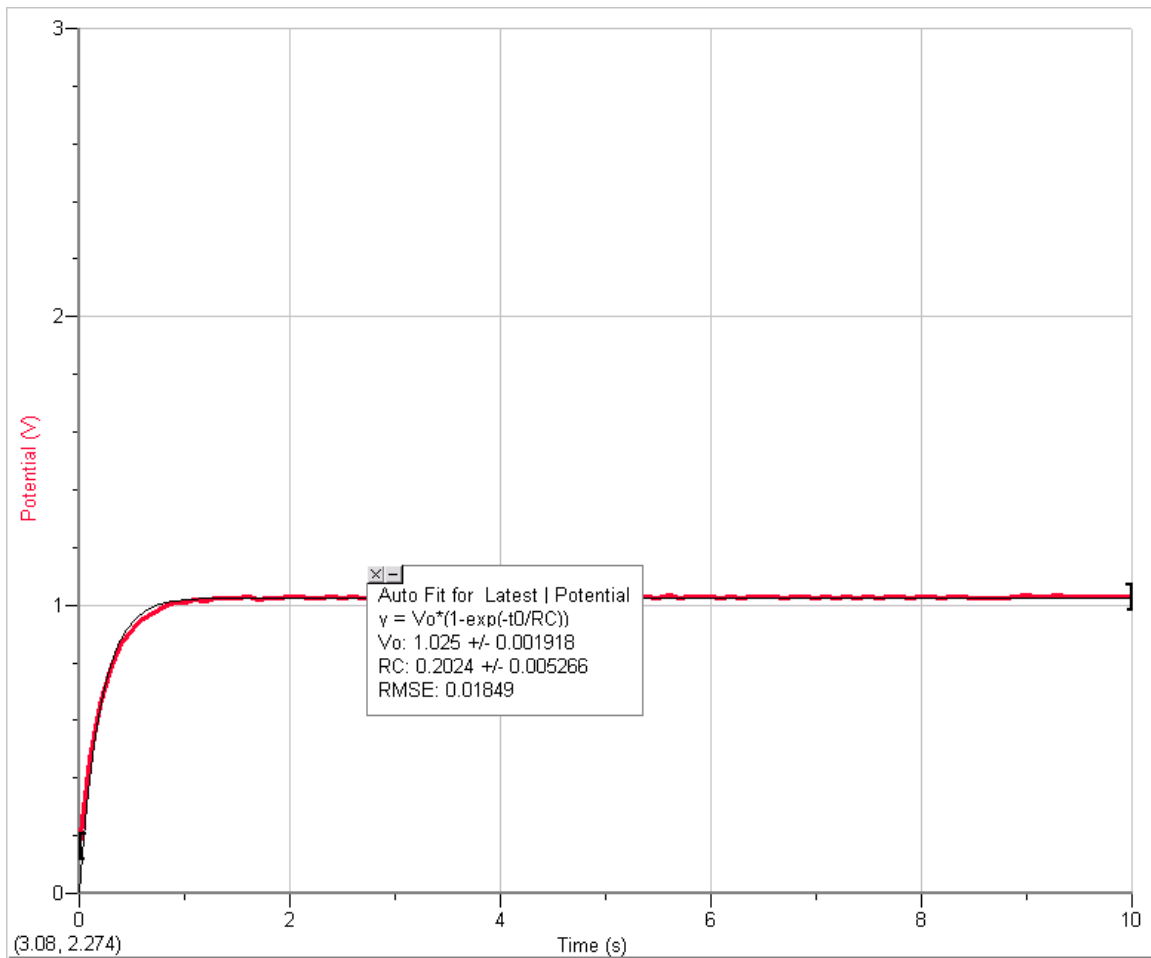

We used Logger Pro to provide a best-fit line for the data captured during the charging of the capacitor.

$$'Potential' = V_o \cdot (1 - \exp(-t_0/RC))$$


Vo [volts]	RC [sec]
1.025 +/- 0.0001918	0.2024 +/- 0.005266

Resistance [ohms]
530 MΩ

$$C = \frac{0.2024 \text{ sec}}{530000 \Omega} = 0.38189 \mu F$$

$$\% \text{ difference} = \frac{0.3824 \mu F - 0.38189 \mu F}{0.3824 \mu F} \times 100\% = 0.133\%$$

Part B2 – Capacitors in Parallel:

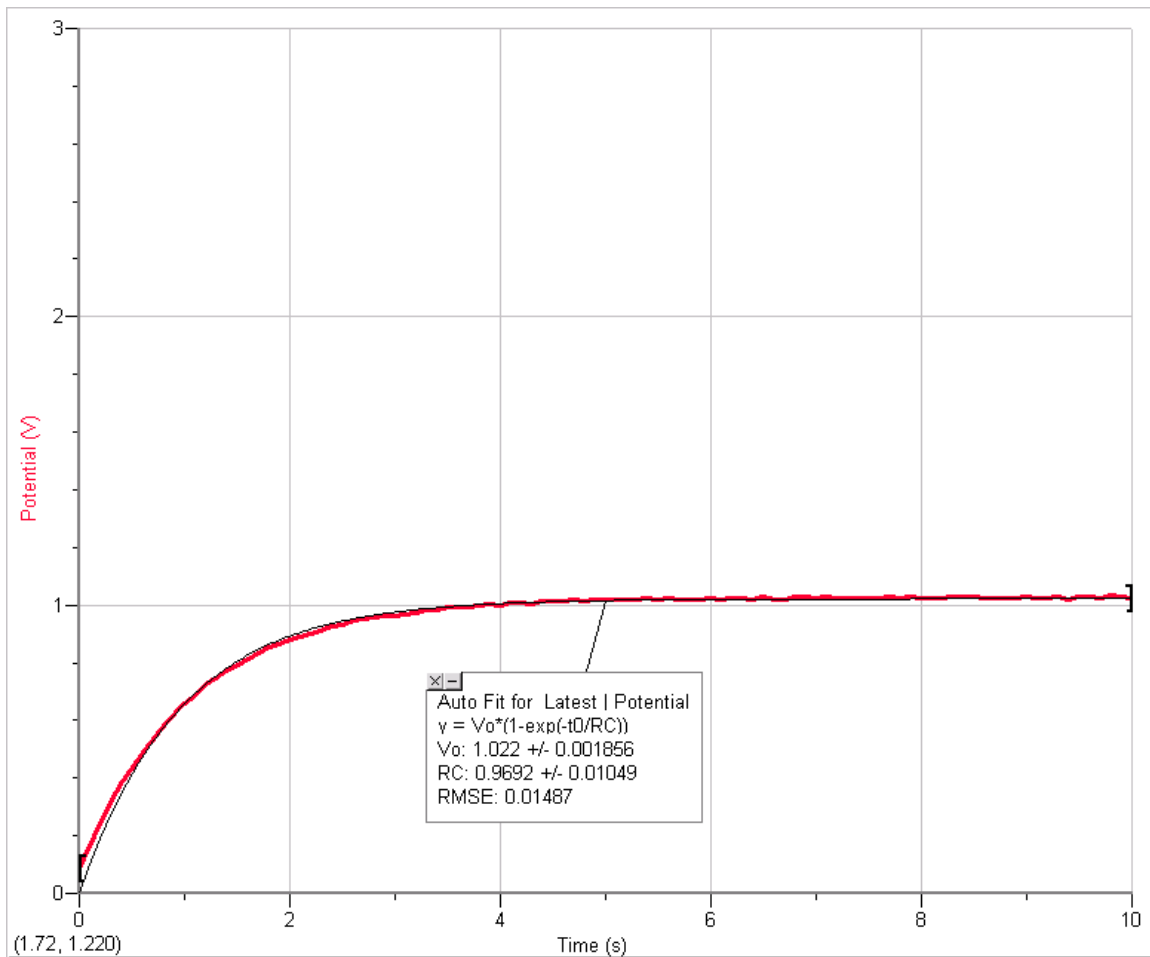

We used Logger Pro to provide a best-fit line for the data captured during the charging of the capacitor.

$$'Potential' = V_o \cdot (1 - \exp(-t_0 / RC))$$

Vo [volts]	RC [sec]
1.022 +/- 0.001856	0.9692 +/- 0.01049

Resistance [ohms]
530 MΩ

$$C = \frac{0.9692 \text{ sec}}{530000 \Omega} = 1.8287 \mu F$$

$$\% - \text{difference} = \frac{1.82425 \mu F - 1.8287 \mu F}{1.82425 \mu F} \times 100\% = 2.439\%$$

Here is an example of a “real world” occurrence of charging/discharging a capacitor. This explains the high-pitched noise (that starts with a low tone and increases to a high tone) you hear after you trigger the flash on a camera.



Capacitors - 8

** NOTE: There are several components of error which could significantly modify the results of this experiment. Some of these are listed below:

- Heat
- Age
- Humidity
- Short circuit
- Fuse
- Bad power supply (recall we used the DMM to attempt to alleviate this problem.)
- Bad connections (in protoboard)
- Insulation
- Length of wire and Gauge accuracy of wire (copper)
- Bad power supply (recall we used the DMM to attempt to alleviate this problem.)
- Buckling, bending, etc... of wire
- Elemental components/material makeup of the wire
- ??

It is recommended that you take these and explain the “*why*” part of each for your results and conclusions sections – and possibly what could have been done (if anything) to minimize the effects of these errors.