

Useful Circuits

Name: Bill Bair

PES 216 Prelab Questions

Lab Station:


**** Disclaimer: This pre-lab is *not* to be copied, in whole or in part, unless a proper reference is made as to the source. (It is strongly recommended that you use this document *only* to generate ideas, or as a reference to explain complex physics necessary for completion of your work.) Copying of the contents of this web site and turning in the material as “original material” is *plagiarism* and will result in serious consequences as determined by your instructor. These consequences may include a failing grade for the particular pre-lab or a failing grade for the entire semester, at the discretion of your instructor. ****

- Calculate the output voltage of a voltage divider with the following:


$$V_{\text{in}} = 10 \text{ V}$$

$$R_1 = 3\text{k}\Omega$$

$$R_2 = 1\text{k}\Omega$$

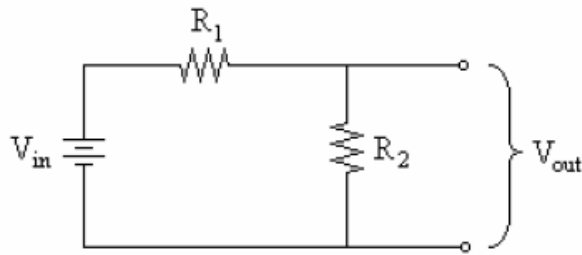

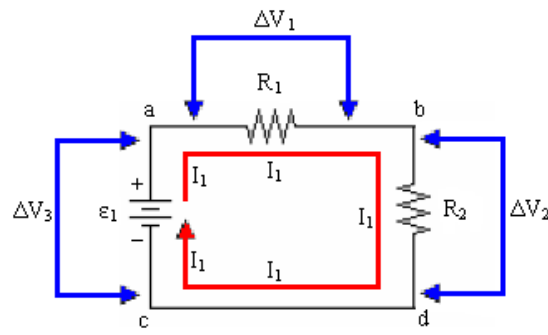
First, let's get this into standard form so we can compare it to the analysis we did for Lab 7. Notice that we've already applied Kirchhoff's Zeroth rule for the current in the circuit:



Next, it is obvious that we need to apply the Loop Rule for the closed loop in the circuit diagram (use Ohm's Law as described at the beginning of the Kirchhoff's Law pre-lab):

We have 1 loop that we need to consider. This loop is (using the letters to describe the loop):

Loop 1 = a-b-d-c-a:

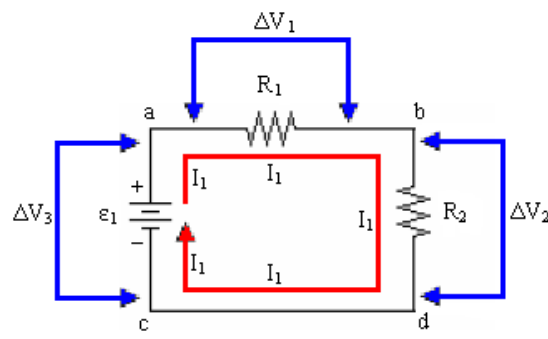

Applying Ohm's Law using the convention set up at the beginning of the pre-lab 7:

From a to b:

$$\underline{\Delta V_1 = -I_1 R_1}$$

From b to d:

$$\underline{\Delta V_2 = -I_1 R_2}$$

From d to c:

$$\underline{\Delta V = 0}$$

From c to a:

$$\underline{\Delta V_3 = +\epsilon}$$

According to the loop rule, the sum of the potential rises and decreases around a closed loop must be zero.

$$\underline{\sum_{i=1}^n \Delta V_i = 0}$$

$$\underline{\sum_{i=1}^4 \Delta V_i = -I_1 R_1 - I_1 R_2 + 0 + \epsilon = 0}$$

$$\underline{-I_1 R_1 - I_1 R_2 + \varepsilon = 0 \text{ (eq. 1)}}$$

Solve the system of equations for the knowns and unknowns:

We are given the following information from the beginning of the problem:

ε	R_1	R_2
10 V	$3 \text{ k}\Omega$	$1 \text{ k}\Omega$

That means that the unknowns are:

$$\underline{I_1}$$

Here is the list of consolidated equations we found using the loop rule and junction rule on the circuit:

$$\underline{-I_1 R_1 - I_1 R_2 + \varepsilon = 0 \text{ (eq. 1)}}$$

First, start by solving equation 1 for I_1 :

$$\underline{-I_1 (R_1 + R_2) + \varepsilon = 0}$$

$$\underline{-I_1 (R_1 + R_2) = -\varepsilon}$$

$$\underline{I_1 = \frac{\varepsilon}{(R_1 + R_2)}}$$

We can now plug in the values of the given information and solve for the numerical value of the current.

$$\underline{I_1 = \frac{10 \text{ V}}{((3\text{k}\Omega) + (1\text{k}\Omega))}}$$

$$\underline{I_1 = \frac{10 \text{ V}}{((3 \times 10^3 \Omega) + (1 \times 10^3 \Omega))} = \frac{10 \text{ V}}{(4000 \Omega)}}$$

$$\underline{I_1 = 0.0025 \text{ A} = 2.5 \text{ mA}}$$

Finally, we can determine the potentials (voltages) across component #2 (where V_{out} is located) by Ohm's Law.

$$\Delta V_2 = -I_1 R_2$$

$$\Delta V_2 = -(2.5 \text{ mA})(1 \text{ k}\Omega) = -(2.5 \times 10^{-3} \text{ A})(1 \times 10^3 \Omega)$$

$$\Delta V_2 = -2.5 \text{ V}$$

Formatted: Left


For a voltage divider, you can use either of the two potential drops (negative delta V's) as your voltage out of the divider, depending on what you need. So say you have an EMF of 10 Volts, like our problem but you only need 2.5 Volts for your circuit to run. Then you would use the potential drop across resistor 2 as your "new" EMF for that circuit. It's like conservation of power! ☺

- Calculate R_1 for the following voltage divider:

$$V_{\text{in}} = 1000 \text{ V}$$


$$V_{\text{out}} = 20 \text{ V}$$

$$R_2 = 1 \text{ k}\Omega$$

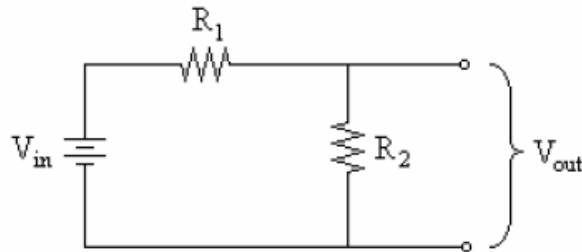

Formatted: Left

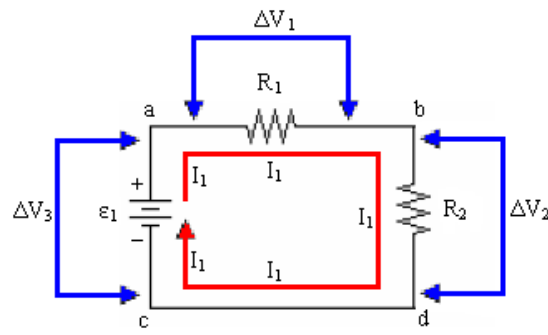Again, setting this up as before, using the standard notation:



It is obvious that V_{in} is ΔV_3 (or simply the EMF) and V_{out} is ΔV_2 . Hence, we are given:

$\underline{\varepsilon}$	$\underline{\Delta V_2}$	$\underline{R_2}$
1000 V	-20 V	1 k Ω

Notice that the sign on the potential drop across resistor two is negative. Recall from the previous problem we had the following from Ohm's Law:

$$\underline{\Delta V_2 = -I_1 R_2}$$

Also, we found an expression for the current:

$$\underline{I_1 = \frac{\varepsilon}{(R_1 + R_2)}}$$

Let's plug the current into the potential drop equation and then solve for R_1 :

$$\underline{\Delta V_2 = -\left(\frac{\varepsilon}{(R_1 + R_2)}\right)R_2 = \frac{-\varepsilon R_2}{R_1 + R_2}}$$

$$\underline{\Delta V_2 (R_1 + R_2) = -\varepsilon R_2}$$

$$\underline{\Delta V_2 R_1 + \Delta V_2 R_2 = -\varepsilon R_2}$$

$$\underline{\Delta V_2 R_1 = -\varepsilon R_2 - \Delta V_2 R_2}$$

$$\underline{R_1 = \frac{-\varepsilon R_2 - \Delta V_2 R_2}{\Delta V_2} = \frac{-R_2 (\varepsilon + \Delta V_2)}{\Delta V_2}}$$

Plugging in the value that we were given,

$$\underline{R_1 = \frac{-(1 \text{ k}\Omega)(1000 \text{ V} + (-20 \text{ V}))}{-20 \text{ V}}}$$

$$\underline{R_1 = \frac{-(1 \text{ k}\Omega)(980 \text{ V})}{-20 \text{ V}} = 49 \text{ k}\Omega}$$

$$\underline{\underline{R_1 = 49 \text{ k}\Omega}}$$


- For the next 2-3 questions assume a Wheatstone Bridge with $A = 1\text{k}\Omega$, $B = 100\text{k}\Omega$ and R set such that the voltmeter is reading 0V . Find the resistance value of X based on the following R values.

$$R = 200\Omega$$

$$R = 4\Omega$$

$$R = 0.1\Omega$$

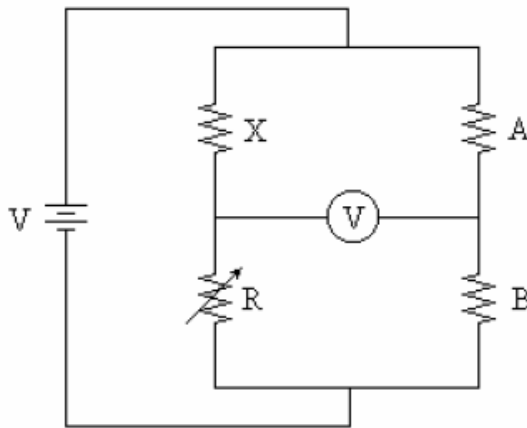** Note that this question is a little flakey. Typically, the values of R are HUGE. (Like on the order of mega-ohms). This may be more believable if the values were kilo-ohms or mega-ohms, but these just seem WAY too small for a typical Wheatstone Bridge. **



From Kirchhoff's Rules (and a lot of algebra) we can show that:

$$X = \frac{RA}{B}$$

For the resistance substitution box set to 200Ω :

$$X = \frac{(200\ \Omega)(1\ \text{k}\Omega)}{(100\ \text{k}\Omega)}$$

$$X = \frac{(200\ \Omega)(1000\ \Omega)}{(100000\ \Omega)} = 2\ \Omega$$

$$\boxed{X = 2\ \Omega}$$

For the resistance substitution box set to 4Ω :

$$X = \frac{(4 \, \Omega)(1 \, k\Omega)}{(100 \, k\Omega)}$$

$$X = \frac{(4 \, \Omega)(1000 \, \Omega)}{(100000 \, \Omega)} = 0.04 \, \Omega$$

$$X = 0.04 \, \Omega$$

For the resistance substitution box set to 0.1 Ω :

$$X = \frac{(0.1 \, \Omega)(1 \, k\Omega)}{(100 \, k\Omega)}$$

$$X = \frac{(0.1 \, \Omega)(1000 \, \Omega)}{(100000 \, \Omega)} = 0.001 \, \Omega$$

$$X = 0.001 \, \Omega$$

Formatted: Left, Indent: Left: 0.25", Line spacing: 1.5 lines, Adjust space between Latin and Asian text, Adjust space between Asian text and numbers